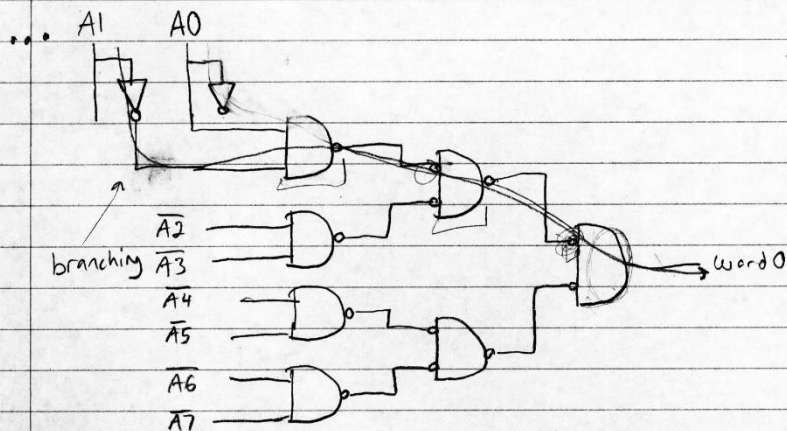



$$H = \frac{f}{v} \quad F = G B H \quad B = 128$$

Design 2:

Using 2 input NANDs / Inverters



Critical Path using available gates:

 

$$G = g_1 g_2 g_3 g_4 g_5 g_6 g_7 \quad P_i: g_2 = g_4 = g_6 \quad g_1 = g_3 = g_5 = g_7$$

$$H = \frac{u}{x}$$

$$F = GBH \quad \text{where } (B = 128 \text{ comes from inverter } x)$$


$$P = P_1 + P_2 + P_3 + P_4 + P_5 + P_6 + P_7 \quad P_2 = P_4 = P_6 \quad P_1 = P_3 = P_5 = P_7$$

$$D_F = (g_1 h_1) + (g_2 h_2) + (g_3 h_3) + (g_4 h_4) + (g_5 h_5) + (g_6 h_6) + (g_7 h_7)$$


$$D = D_F + P \quad \hat{f} = \sqrt[7]{F}$$

Design 3:

 Using 4-input NANDS, 2-input NANDS, and Inverters



Critical path:

 

$$G = g_1 \cdot g_2 \cdot g_3 \cdot g_4 \cdot g_5 \quad H = \frac{\text{count}}{y} \quad B = 128 \text{ (from gate 1)}$$

$$P = P_1 + P_2 + P_3 + P_4 + P_5 \quad f = \sqrt[5]{F}$$

$$D_F = (g_1 h_1) + (g_2 h_2) + (g_3 h_3) + (g_4 h_4) + (g_5 h_5) \quad D = D_F + P$$

Design 1 Calculations:

$$G = g_2 g_3 g_4 g_5 = 1.465 * 0.83 * 1 * 0.83 = 1.009$$

$$P = p_2 + p_3 + p_4 + p_5 = 1.57 + 2.09 + 1 + 2.09 = 6.75$$

$$H = \frac{512}{3}$$

$$B = 64$$

$$F = GHB = 11020.97$$

$$f' = F^{\frac{1}{4}} = 10.25$$

$$D = Nf' + P = 47.73$$

Design 2 Calculations:

$$G = g_2 g_3 g_4 g_5 g_6 g_7 = 1.465 * 1 * 1.465 * 1 * 1.465 * 1 = 3.14$$

$$P = p_2 + p_3 + p_4 + p_5 + p_6 + p_7 = 1.57 + 1 + 1.57 + 1 + 1.57 + 1 = 7.71$$

$$H = \frac{512}{3}$$

$$B = 64$$

$$F = GHB = 34297.173$$

$$f' = F^{\frac{1}{6}} = 5.70$$

$$D = Nf' + P = 41.91$$

Design 3 Calculations:

$$G = g_2 g_3 g_4 g_5 = 2.155 * 1 * 1.465 * 1 = 3.157$$

$$P = p_2 + p_3 + p_4 + p_5 = 2.86 + 1 + 1.57 + 1 = 6.43$$

$$H = \frac{512}{3}$$

$$B = 16$$

$$F = GHB = 8621$$

$$f' = F^{\frac{1}{4}} = 9.6358$$

$$D = Nf' + P = 44.9732$$

We are choosing design 3 for several reasons. First of all the g value for NOR seems incorrect (0.83) as it is less than that of an inverter. This caused our G value for Design 1 to be skewed. Looking at Design 2 and 3, which did not use NOR gates, we can see that Design 2 has a lower delay, however it utilizes 6 stages and many more gates. This will result in more area required for the layout which is undesired. This led us to choose design 3, which had a slightly larger delay but fewer stages, meaning a more compact layout.